

California State University Sacramento
Electrical and Computer Science Department

EEE 108L Lab - Section 05
Laboratory Experiment Number 7: Lab Report

BJT Application
Common-Emitter Biasing and Amplification
Fundamentals

Author: John Jimenez
Lab Partner: Jonas

Table of Contents

Abstract	3
Part 1: Preliminary Calculations.....	3
STEP 1: Find the value of VBB.....	3
STEP 2: What percentage would the collector current increase?.....	4
STEP 3: What is the new collector current and by what percentage did it change?.....	4
STEP 4: Find an approximate expression for Vc/Vb.....	5
Part 2: Spice Simulations.....	5
STEP 5: Construct Figure 1 Circuit.....	5
STEP 6: Edit circuit by increasing B by 50%.....	6
STEP 7: Increase temp and record results.....	6
STEP 8: Set up DC Sweep.....	7
Part 3: Laboratory Experiment.....	8
STEP 9: Construct the Circuit from figure 1.....	8
STEP 10: Add components to circuit.....	9
STEP 11: DC Coupling triangle waveform.....	10
STEP 12: Increase AC amplitude.....	10
STEP 13: Replace VBB and RBB with a voltage divider with 2 resistors.....	11
CONCLUSION:	13
ITEM 1:	13
ITEM 2:	13
ITEM 3:	13
ITEM 4:	13
ITEM 5:	13
ITEM 6:	13
ITEM 7:	13

ADDENDUM

Abstract

For this laboratory experiment we are experimenting on factors affecting the DC bias of a common-emitter amplifier stage. When the stage is biased, the base voltage will be driven with an AC signal to illustrate principles of common-emitter amplifier operation. In this lab the SPICE Simulations and the experimental portion of the circuit will use 2N2222 small-signal amplifier transistor.

Part 1: Preliminary Calculations

STEP 1:


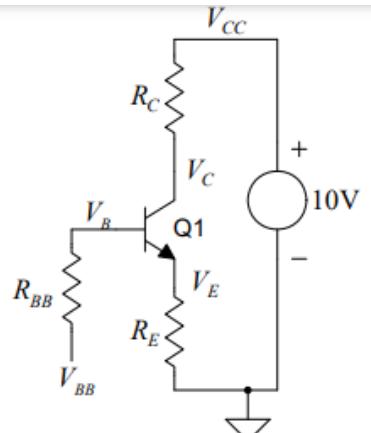


Figure 1. BJT Bias Circuit

①

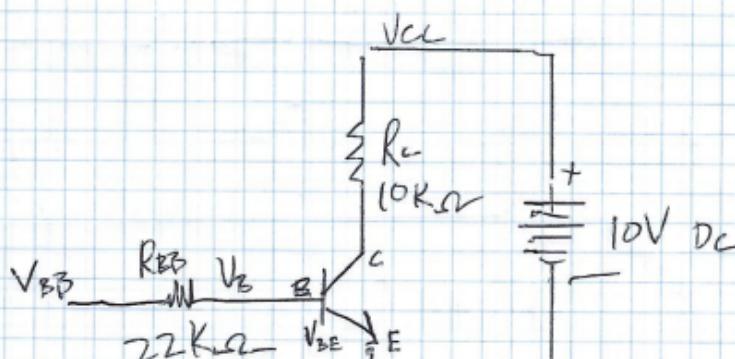

FIND V_{BB} THAT RESULTS
IN $I_C = 0.5 \text{ mA}$

$$I_B = I_C / \beta = 0.5 / 150 =$$

$$I_B = 3.33 \times 10^{-6} \text{ A or } 3.33 \mu\text{A}$$

VOLTAGE DROP ACROSS
 $R_{BB} = 3.33 \times 10^{-6} \cdot 22 \text{ k}\Omega$
 $= 0.0733 \text{ V}$


$$V_{BB} = (3.33 \mu\text{A})(22 \text{ k}\Omega) + 0.7 \text{ V} + 0.5 \cdot 1 \text{ k}\Omega = 1.2733 \text{ V}$$

STEP 2:

(2)

$$1.2733V = I_B \cdot 22k\Omega + 0.7V + I_B \cdot 225 \cdot 1k$$

$$0.5733V = 247k\Omega \cdot I_B$$

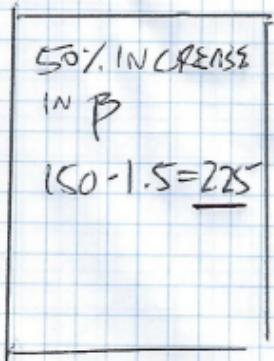

$$I_B = 2.32\mu A$$

$$I_C = \cancel{2} 0.522mA$$

$$\frac{0.522mA}{0.5mA} = 1.044$$

I_C CHANGES BY 4.4%

STEP 3:

(3)

$$V_{BE} = 1.2733V$$

$$V_{BE} = 0.7V \cdot \left(\frac{-2mA}{C}\right) \left(\frac{-40V}{C}\right) = 0.62V$$

$$\beta = \cancel{150} \cdot \frac{(1.5 + 2.5)}{40}$$

β CHANGES BY $(0.0125) \left(\frac{40}{C}\right) = 0.5$
50%

$$\beta = 225$$

$$1.2733 = I_B \cdot 22k + 0.62 + I_B \cdot 225 \cdot 1k\Omega$$

$$0.6533 = I_B \cdot 22k + I_B \cdot 225,000$$

$$0.6533 = I_B \cdot 247,000$$

$$I_B = 2.6447 \times 10^{-6}, \quad 2.64\mu A$$

$$I_C = 2.64\mu A \cdot 225 = 0.595mA$$

$$\frac{0.595mA}{0.500mA} = 1.19 \quad 19\% \text{ INCREASE}$$

IN I_C

STEP 4:

$$\textcircled{4} \quad \frac{\Delta V_C}{\Delta V_B} = \frac{V_{CC} - I_C R_C}{V_{BE} + I_E R_E} \quad I_E = I_C \cdot \frac{\beta}{\beta+1} \approx I_C$$


$\nearrow \Delta V_B$

CHANGE


$$\frac{\Delta V_C}{\Delta V_B} = \frac{V_{CC} - I_C R_C}{V_{BE} + I_E R_E} = -\frac{R_C}{R_E}$$

Part 2: Spice Simulations


STEP 5: B = 150, I = 274.9uA

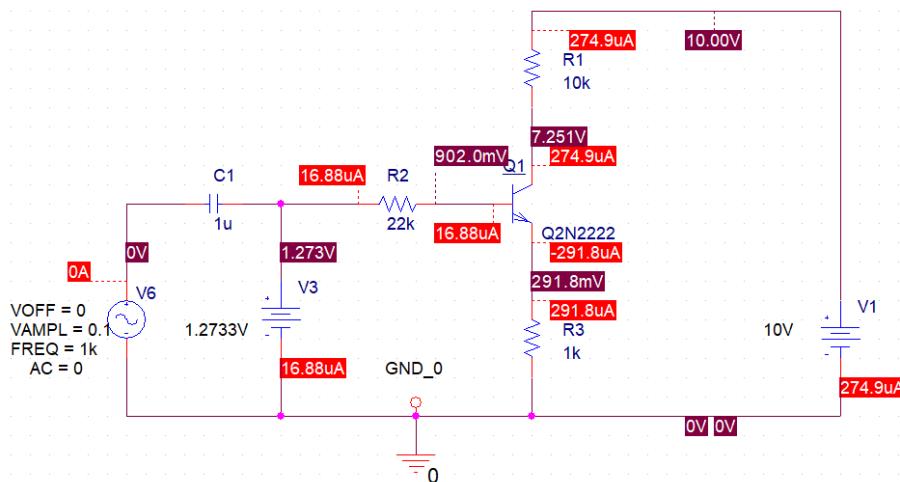

Current Trace

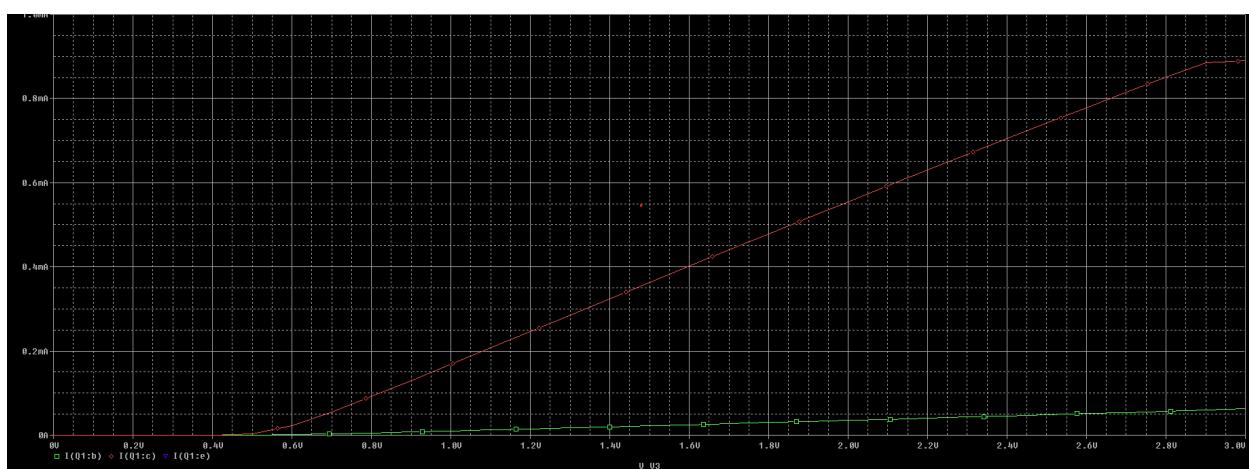


STEP 6: switch B to 225

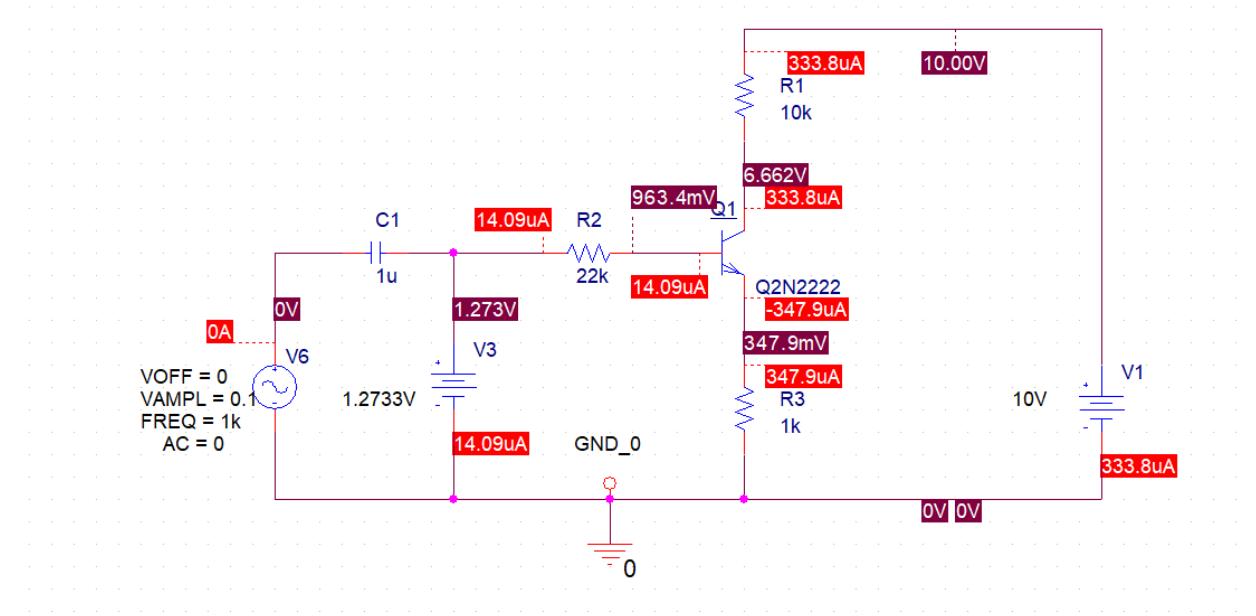


We found a 17% increase after increasing the value of Beta.

STEP 7: Circuit bias point at 40 degrees C. Also Beta value = 150, I = 284.7uA.

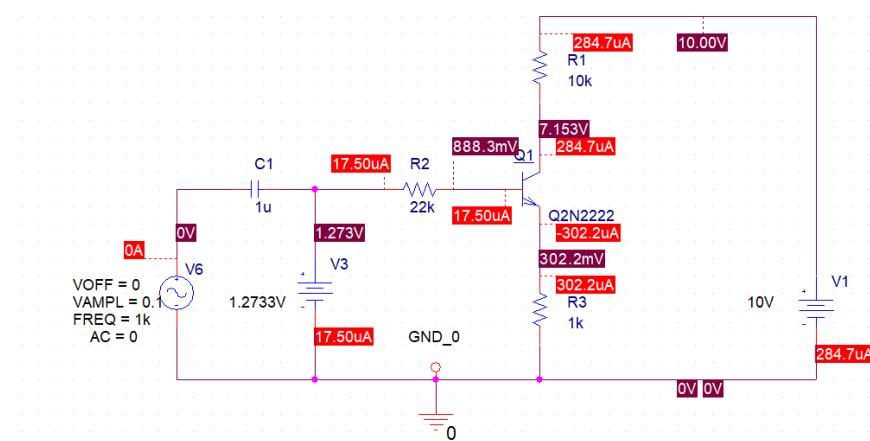We found that there was only a slight increase of 3% = $(284.7 - 274.9)/284.7 = 0.034 \times 100$



STEP 8:

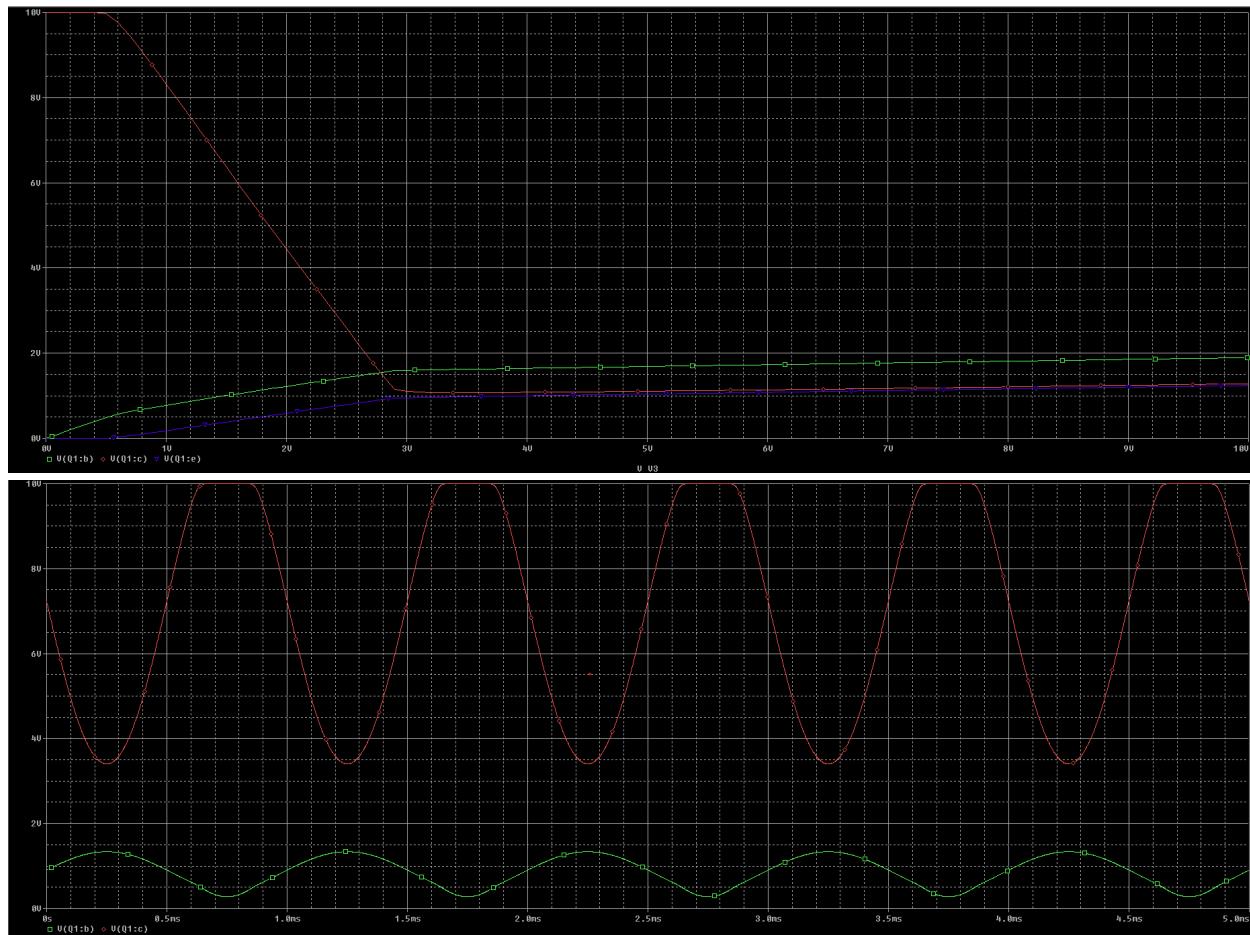


Part 3: Laboratory Experiment

STEP 9:

$$V_{cc} = 10V$$

$$RC = 10k\Omega$$


$$R_{bb} = 22k\Omega$$

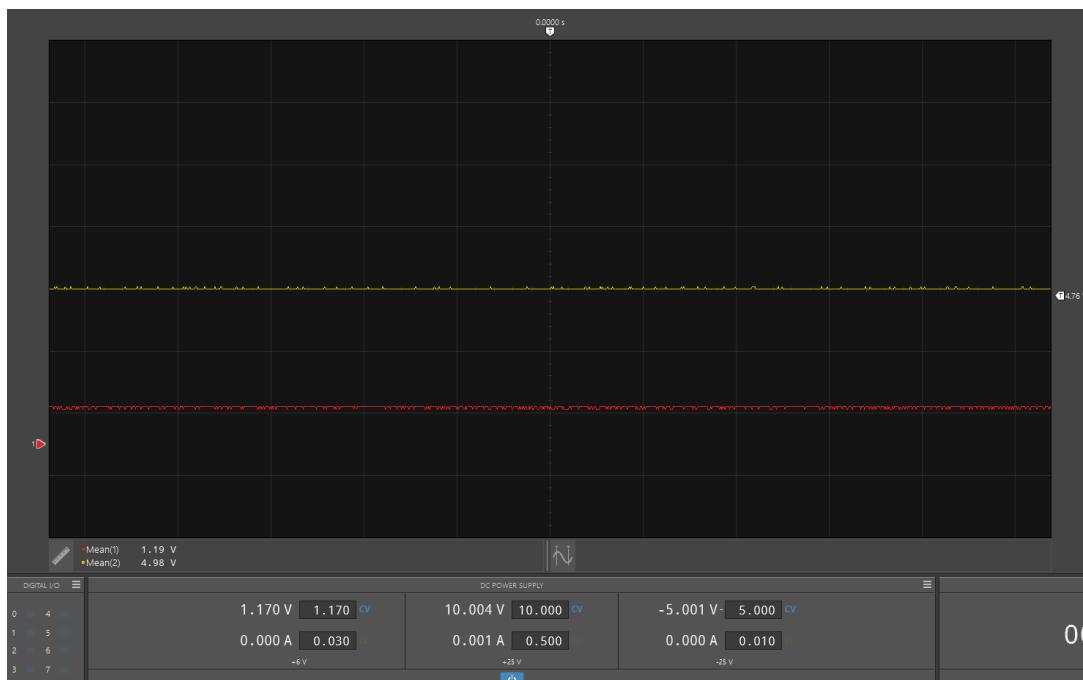

V_{BB}	V_B	V_c	$I_c = \frac{V_{cc} - V_c}{R_c}$	LARGE SIGNAL GAIN
0	0.1V	9.8V	2×10^{-5}	$A_{Vc} = 4.2$
0.5	0.42V	9.8V	2×10^{-5}	$A_{VB} = 0.45$
1	0.8V	6.4V	3.6×10^{-4}	≈ 9.35
1.5	1.25V	2.19V	7.81×10^{-4}	
2	1.42V	1V	9×10^{-4}	
2.5	1.43V	1.02V	8.98×10^{-4}	
3.	1.59V	1.03V	8.97×10^{-4}	


When $I_c = 0.5mA$
when the $V_{BB} = 1.170V$

STEP 10: Cap= 22uF

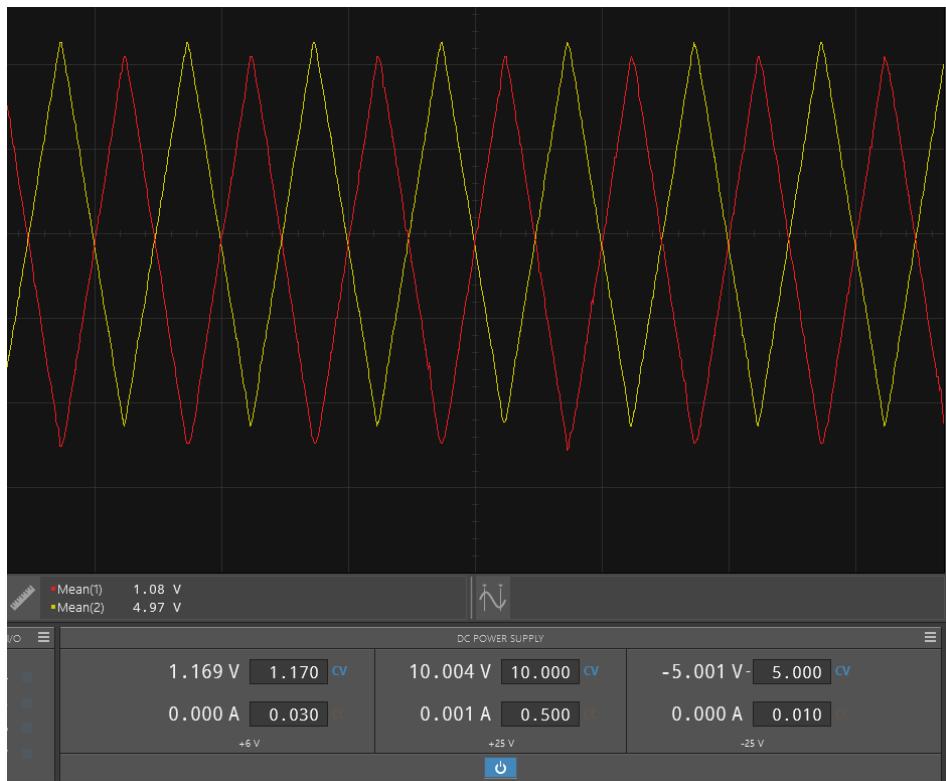


$$\text{Small signal gain} = V_c/V_b = 914\text{mV}/91\text{mV} = 10.04$$

STEP 11:

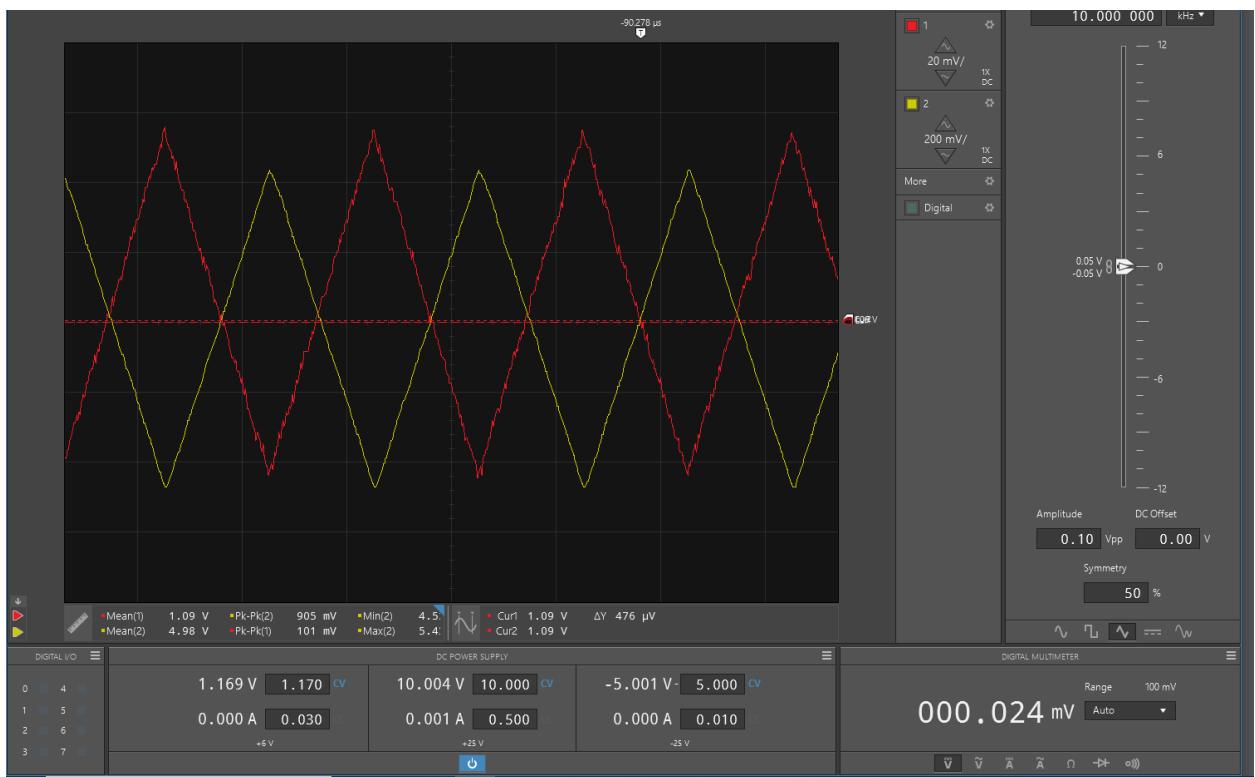

STEP 12:

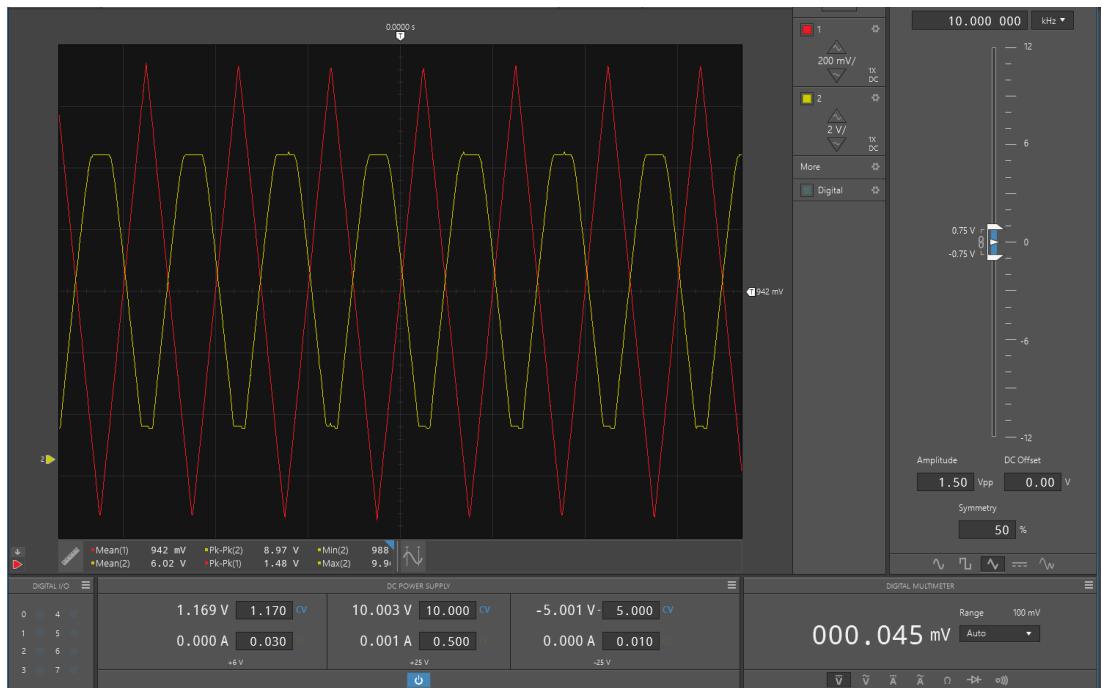

Max = 9.9 supply V, Min = 0.916 emitter V

STEP 13: Replace VBB and the RBB


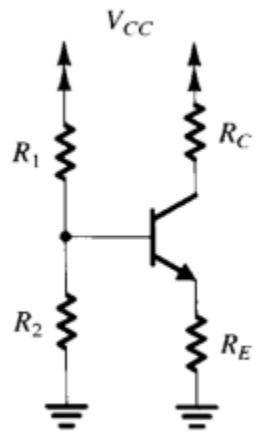


Figure 3. Alternate Input Bias Circuit

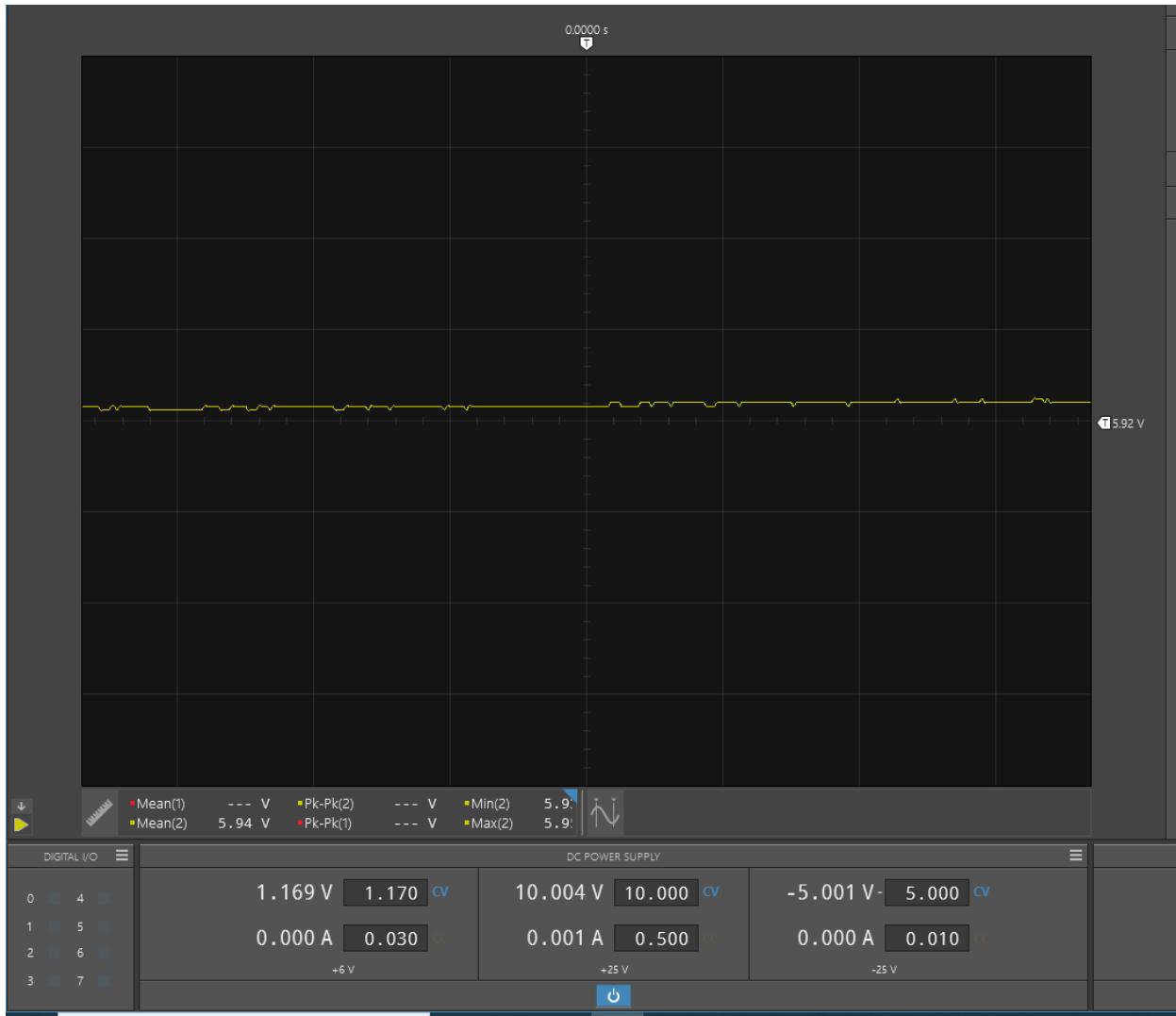

Lab 7

Part 13 continuation

$$\frac{1.17R_1}{10}$$

$$I_2 = \frac{1.17R_1(0.883)}{10}$$

$$22k = \frac{R_1 + R_2}{R_1 + R_2}$$

$$22k = \frac{R_1 \cdot (1.17R_1(0.883))}{10}$$

$$R_1 + \frac{(1.17R_1(0.883))}{10}$$

$$22k = \frac{R_1 \cdot 0.103R_1}{1R_1 + 0.103R_1}$$

$$22k = \frac{0.103R_1}{1.103R_1}$$

$$22k = 0.093R_1$$

$$R_1 = 23554 \quad \text{or } 1881034 \Omega$$

$$R_2 = \quad \text{or } 25k\Omega$$

$$I_C = \frac{10 - 5.93}{10k} = 0.407$$

$$\text{Solve} \rightarrow 0.5 - 0.407 = \frac{0.093}{0.5} \times 100 = 18.6\%$$

For percent error

CONCLUSION:

ITEM 1: What spice does differently is having different Beta values. And VBE is not easy to find as it has more specific calculations that just do not appear on spice.

ITEM 2: It is not septical to change. This is because the Tolerance to B is strong.

ITEM 3: Sor the changes after the change in temp was basically non existent as the change was only 3.4%

ITEM 4: The current gain which is $(V_{cc}-V_c)/R_c = I_c$

ITEM 5: We can conclude that the small signal gain was about 9.35

ITEM 6: If comparing step 10 small signal gain to the slope of the transfer in step 9, we see that the difference is only $10.04 - 9.35 = 0.69$

ITEM 7: The shape of the clipping seen in step 12 compared to the Vc in step 8. We see that They clip around 1.5VPP at around 9.9V.