

California State University Sacramento  
Electrical and Computer Science Department

**EEE 108L Lab - Section 05**  
**Laboratory Experiment Number 8: Lab Report**

**A Common-Emitter Design Exercise**

**Author:** John Jimenez  
**Partner:** Jonas Villegas

## **Table of Contents**

<b>Abstract .....</b>	<b>3</b>
<b>Part 1: Preliminary Calculations .....</b>	<b>3</b>
STEP 1A: Show that a change in the collector current will not change the gain.....	3
STEP 1B: How does the gain reduce when RL is finite.....	4
<b>Part 2: Spice Simulations.....</b>	<b>4</b>
STEP 2: Construct figure 1 Circuit on SPICE.....	4
STEP 3: AC sweep to determine midband freq and midband V gain.....	5
STEP 4: Simulate to check for output voltage swing.....	5
STEP 5: Simulate to check for input resistance.....	6
STEP 6: .....	6
STEP 7: Investigate the frequency response.....	7
<b>Part 3: Laboratory Experiment.....</b>	<b>8</b>
STEP 8: Construct figure 1 Circuit.....	8
STEP 9: Determine midband range and midband small-signal gain.....	9
STEP 10: Determine the maximum output signal level.....	9
STEP 11: Frequency sweep to find the lower -3db frequency.....	10
<b>CONCLUSION: .....</b>	<b>11</b>
ITEM 1: .....	11
ITEM 2: .....	11

ADDENDUM

## Abstract

For this laboratory experiment is a design exercise that involves a common-emitter amplifier. In this lab we were given the set CE7 which contained the following. In this lab we will also be using 2n2222 BJT.

Set CE7	Load Resistance	$R_L$	1k	$\Omega$	$\pm 5\%$
	Voltage gain	$v_o/v_s$	2	V/V	$\pm 10\%$
	Power supply voltage	$V_{CC}$	5	V	$\pm 5\%$
	Minimum swing capability	$v_{out \max}$	0.42	V <sub>pp</sub>	$\geq$ spec.
	Input Resistance	$R_{in}$	15k	$\Omega$	$\geq$ spec.


## Part 1: Preliminary Calculations

### STEP 1A:

Assuming that,

$$REA = 0$$

$$RL = \infty$$

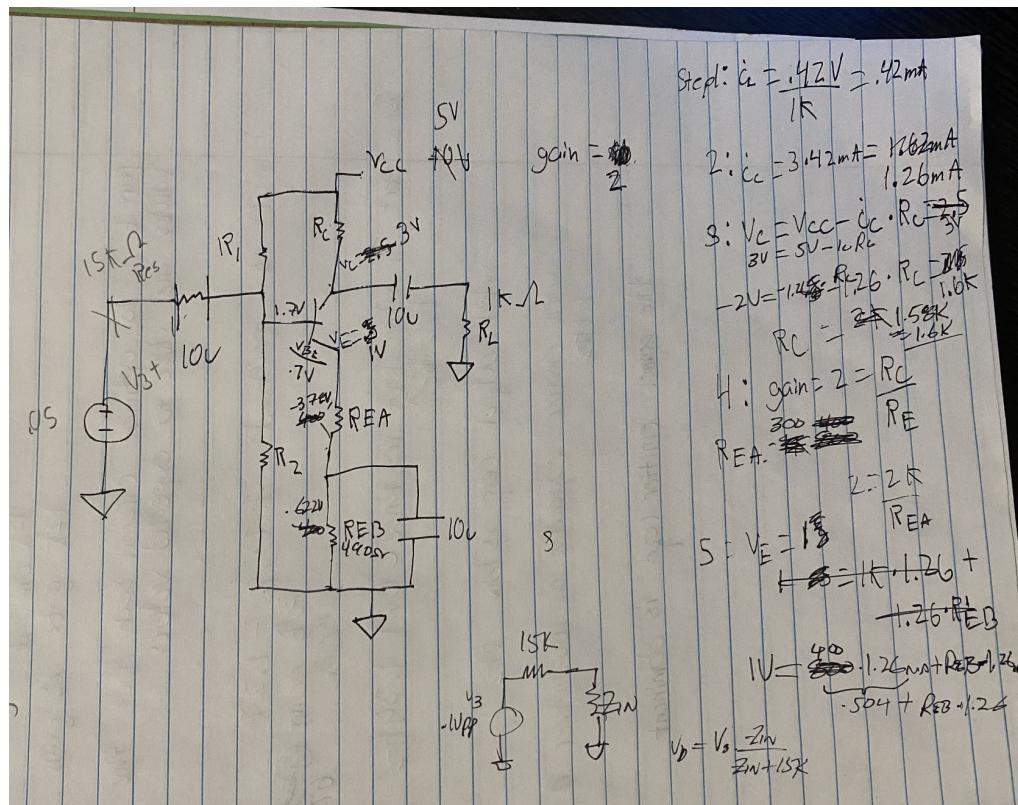

### STEP 1B:

$$1: i_L = \frac{.42V}{1k} = .42mA$$

$$2: i_L = 1.26mA$$

$$3: V_L = V_{CC} - i_L \cdot R_C = 2.984$$

$$4: \text{gain} = 2 = \frac{R_C}{R_E}$$

$R_EA$

$$5: V_E = 1V = 1.26mA \cdot 300 + 1.26mA \cdot R_{EB}$$

$$R_{EB} = 490$$

~~$V_B = V_E$~~

$$6: V_B = V_E + V_{BE} = 1V + .7 = 1.7$$


$$V_B = 1.7V = \frac{R_2}{R_1 + R_2} \quad R_1 = 8.8k$$

$$R_2 = 21.4k$$


$$R_{in} = ISK = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

### Part 2: Spice Simulations



### STEP 2:

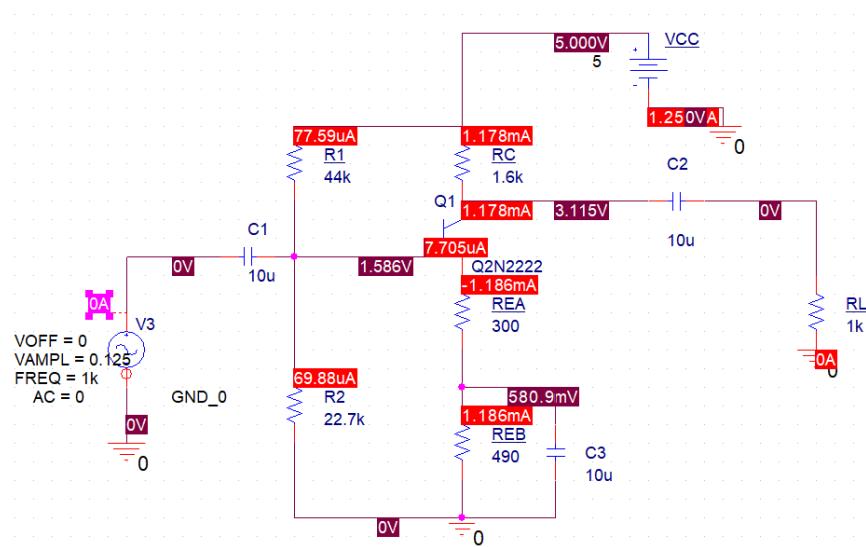


### STEP 3: AC sweep

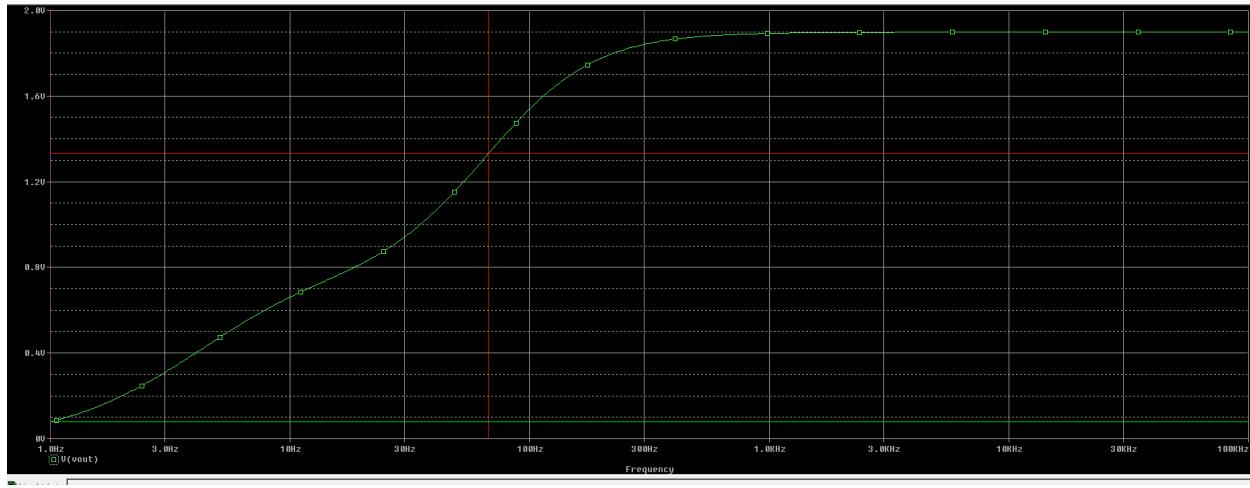

### STEP 4:

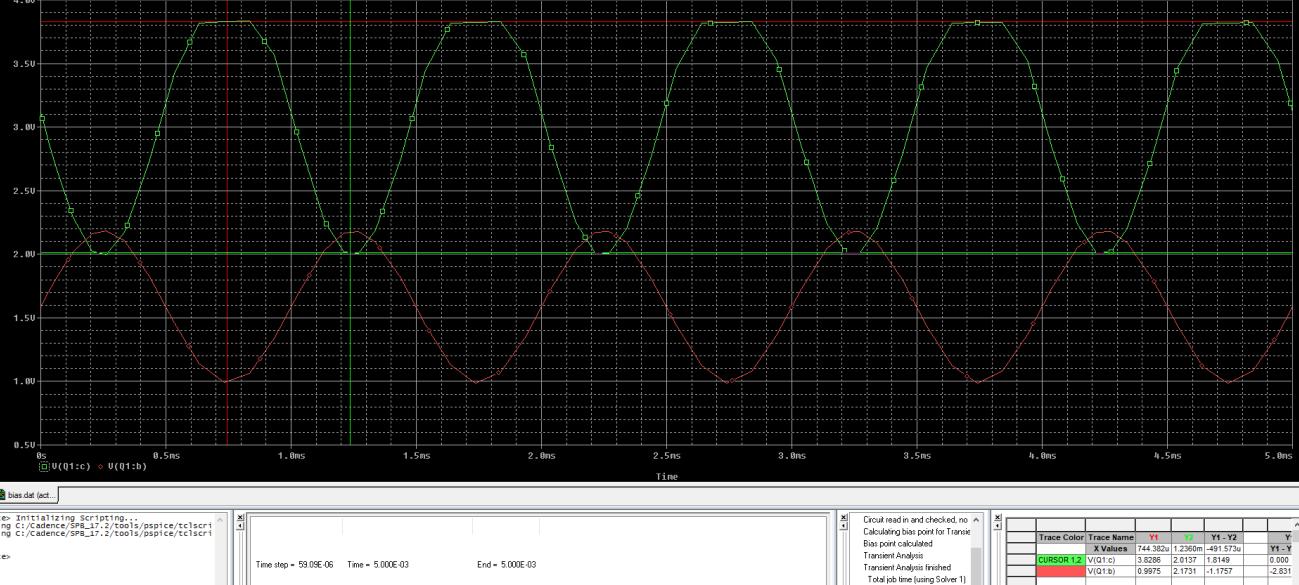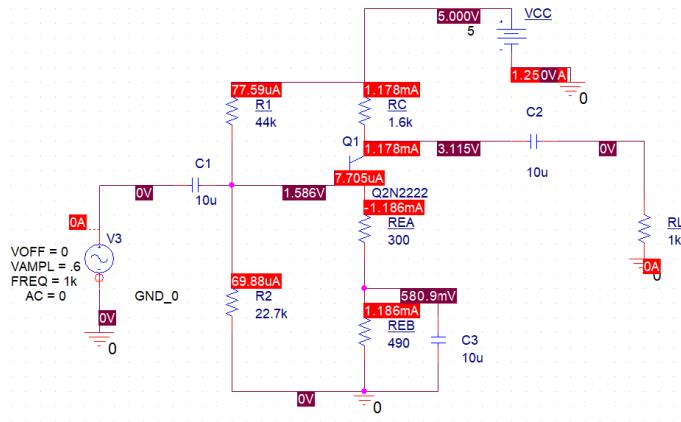

## STEP 5:

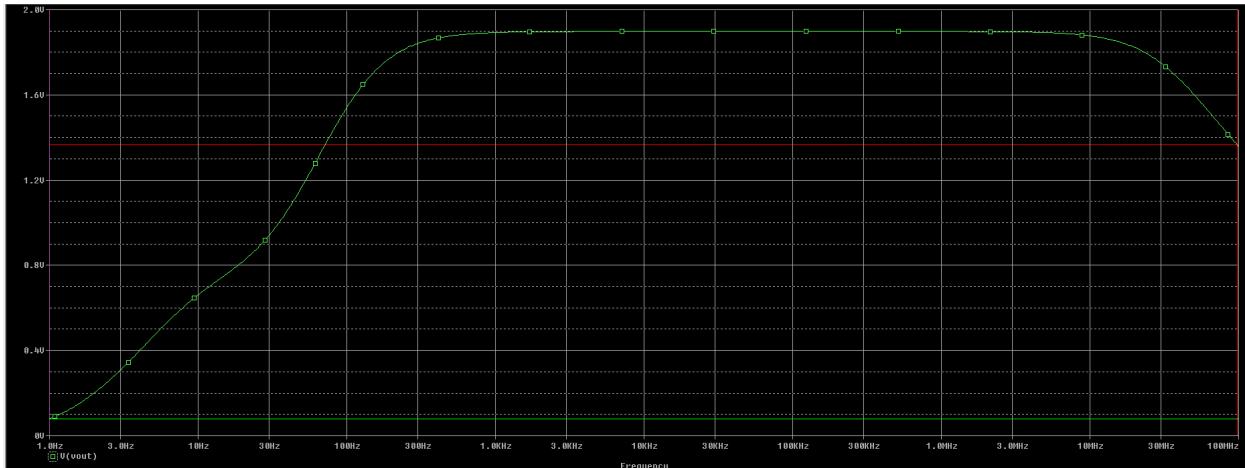


## STEP 6:

$$VB = VE + VBE = 1V + 0.7V = 1.7V$$


$$VB = 1.7V$$

$$R_{in} = 15k$$

New schematic:

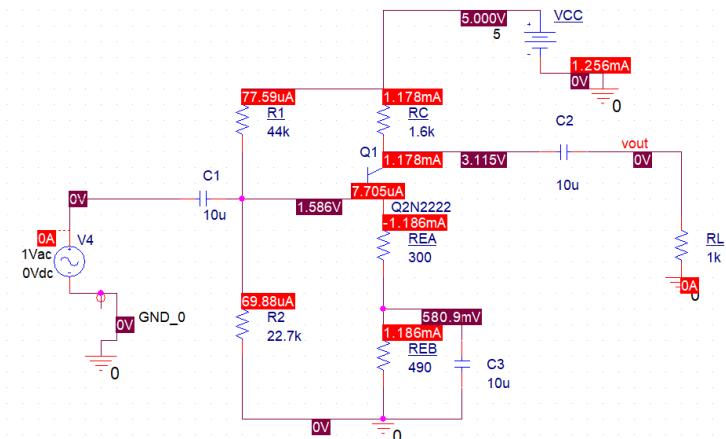

## STEP 7:

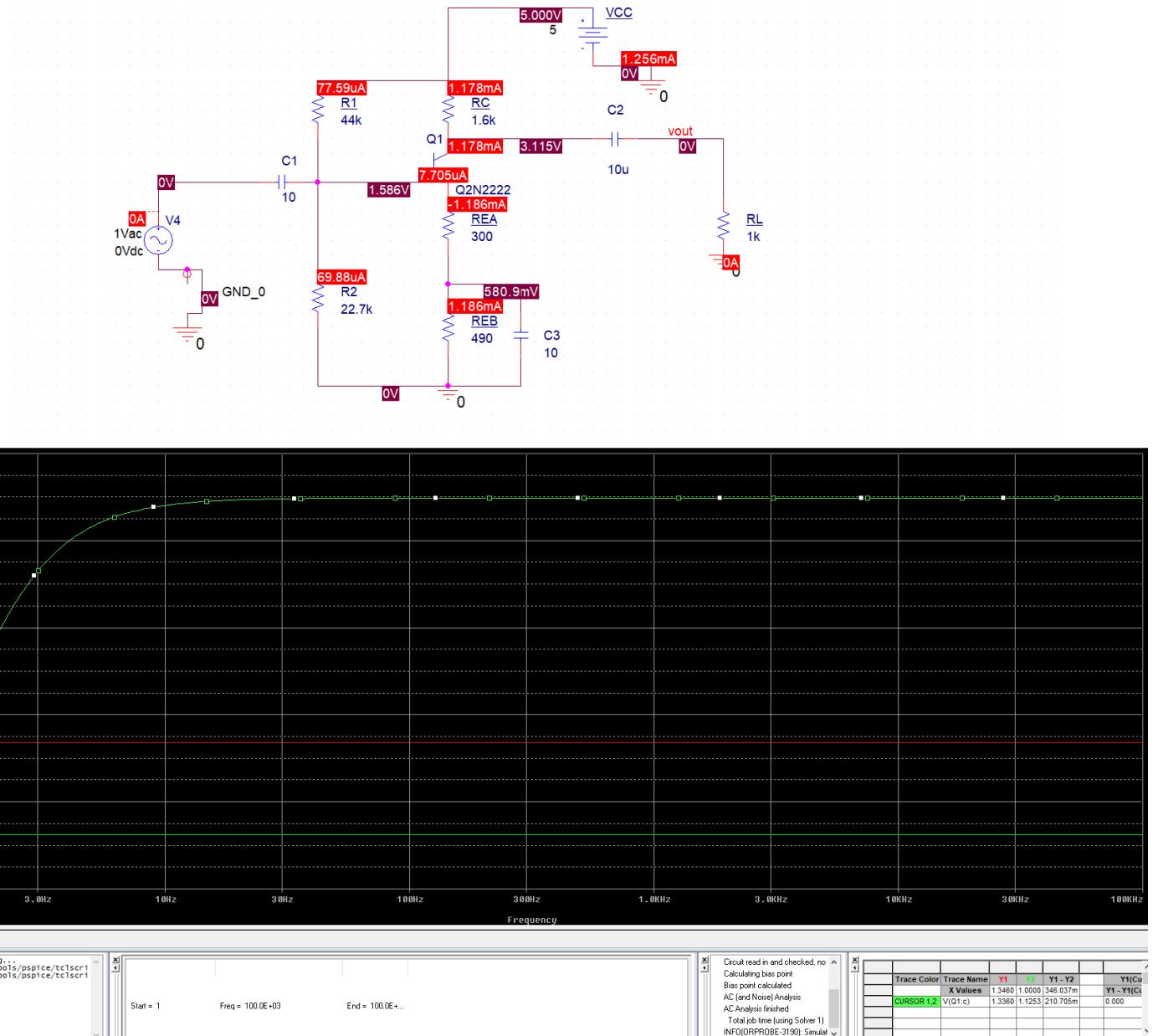

## Part 3: Laboratory Experiment

### STEP 8:

The values of the circuit components include:

$$R_1 = 43\text{k}\Omega$$

$$R_2 = 22\text{k}\Omega$$

$$REB = 470\Omega$$

$$R_C = 1.6\text{k}\Omega$$


$$REA = 300\Omega$$

$$RL - 1\text{k}\Omega$$


$$C_1 = 10\text{ }\mu\text{F}$$

$$C_2 = 4.7\text{ }\mu\text{F}$$


$$C_3 = 4.7\text{ }\mu\text{F}$$

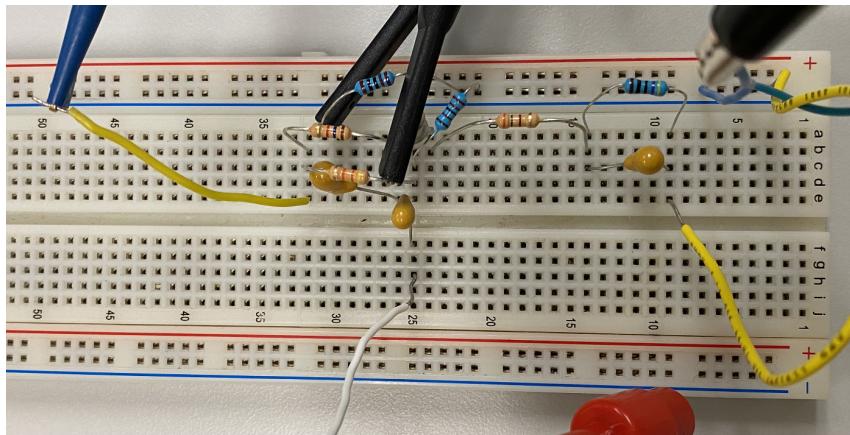

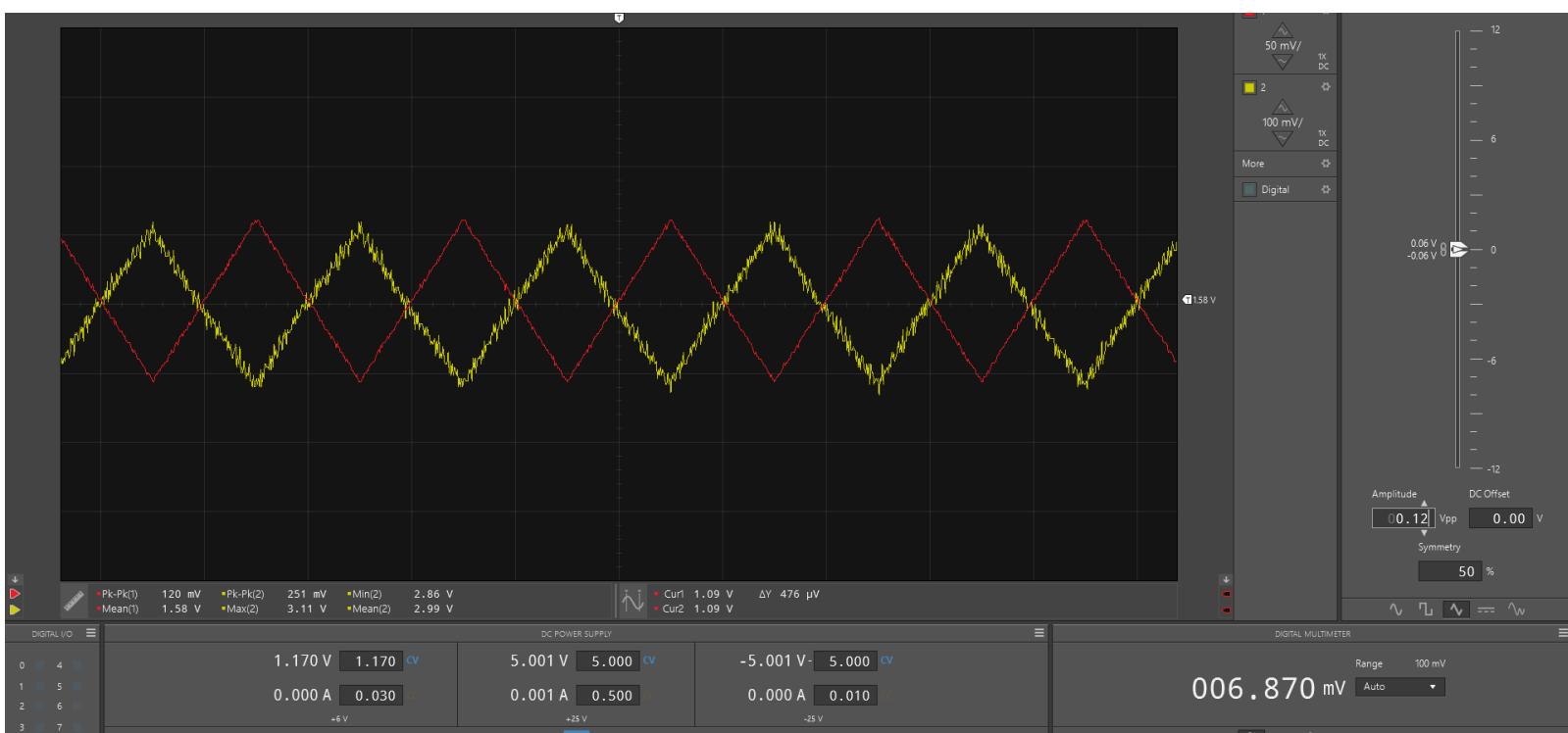
$$\text{Collector current} = 2.99/(1.6 \times 10^3) = 1.86\text{mA}$$





## STEP 9:

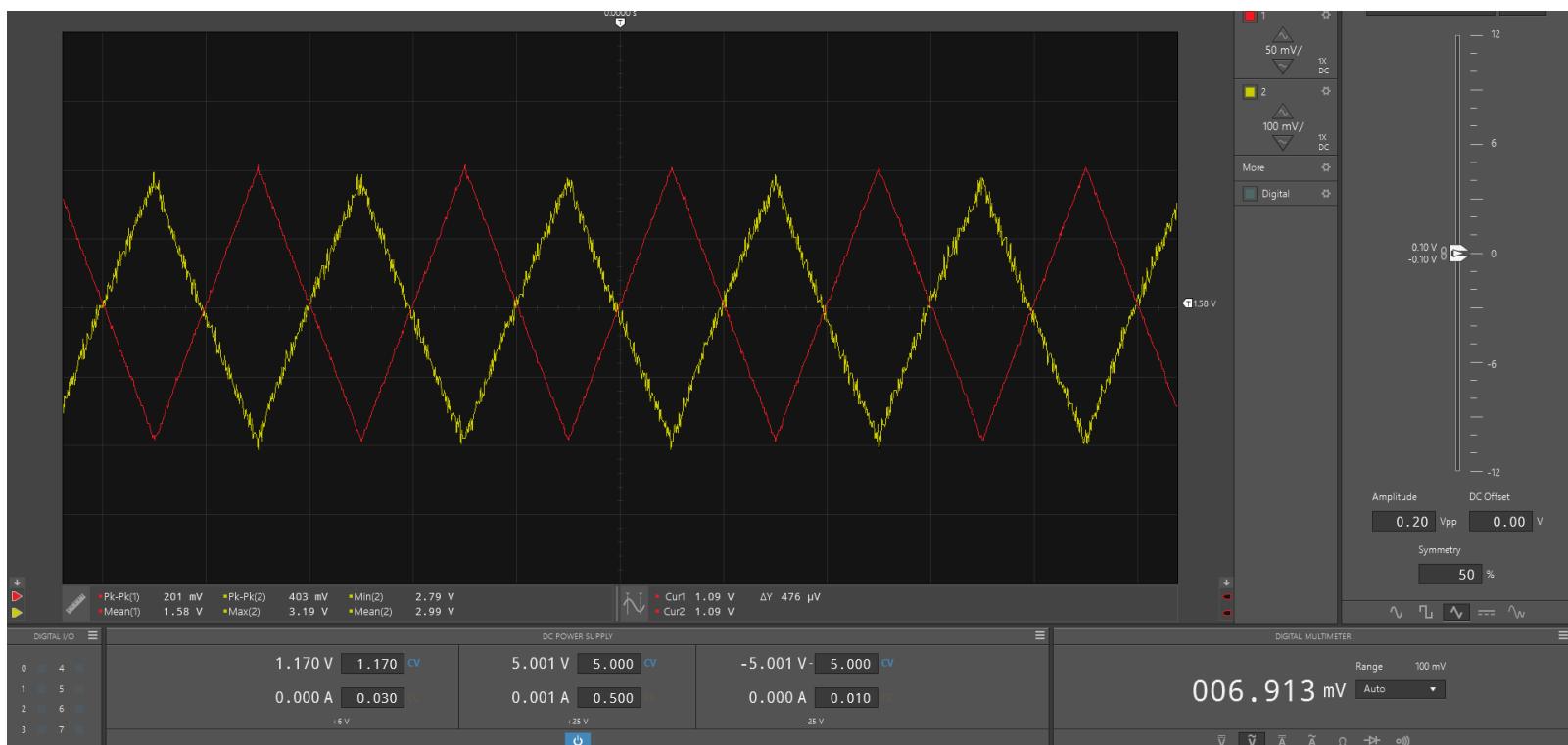

## STEP 10:

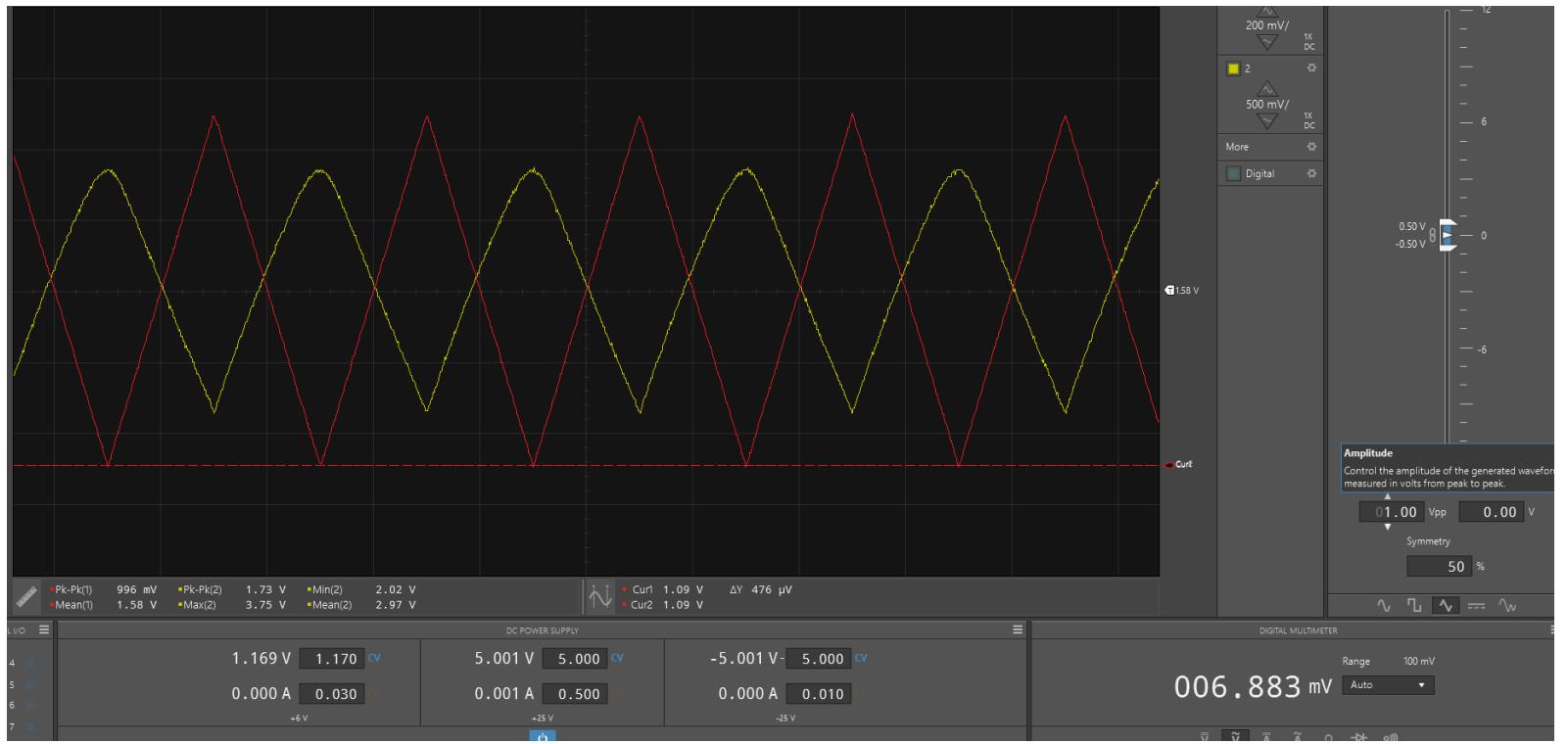


## STEP 11:

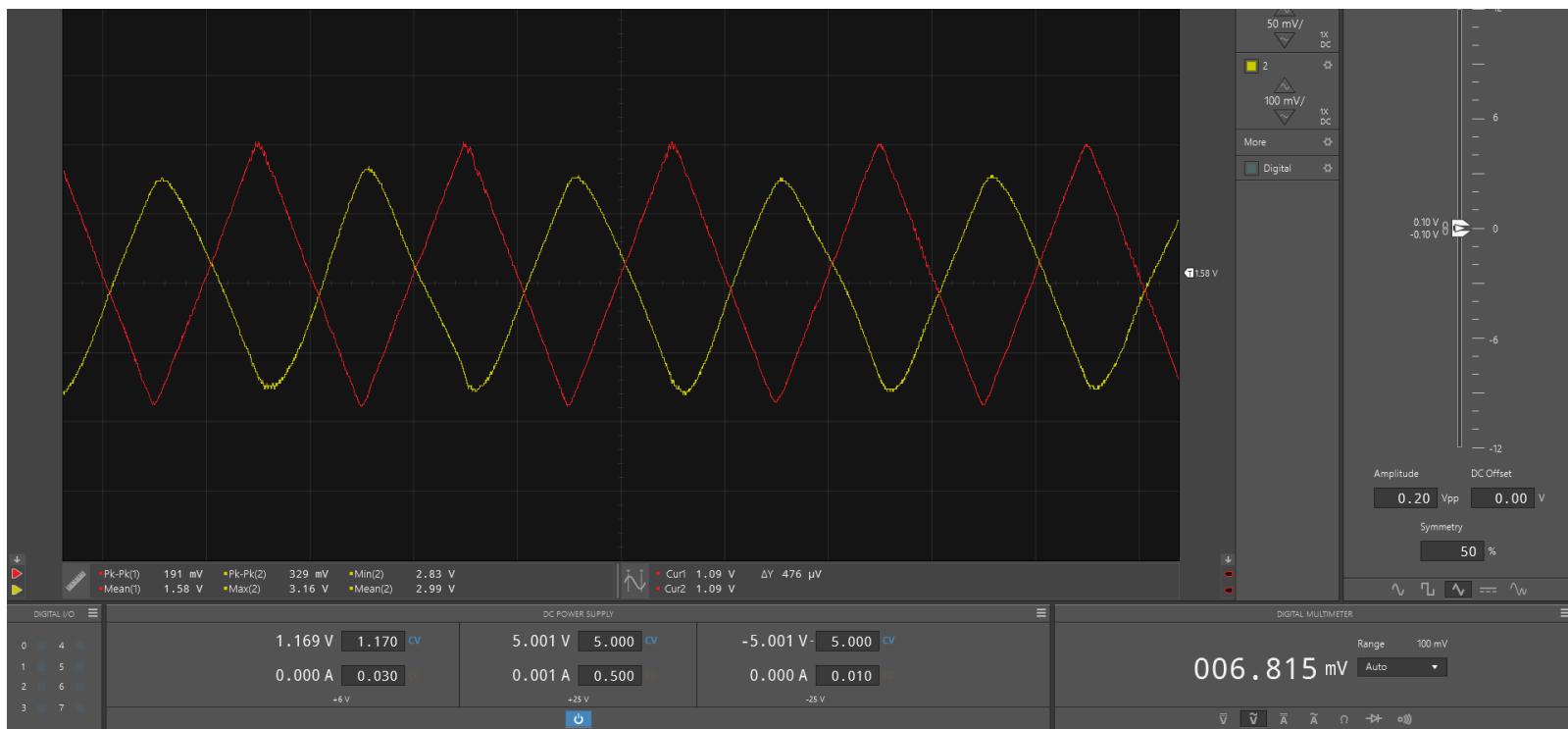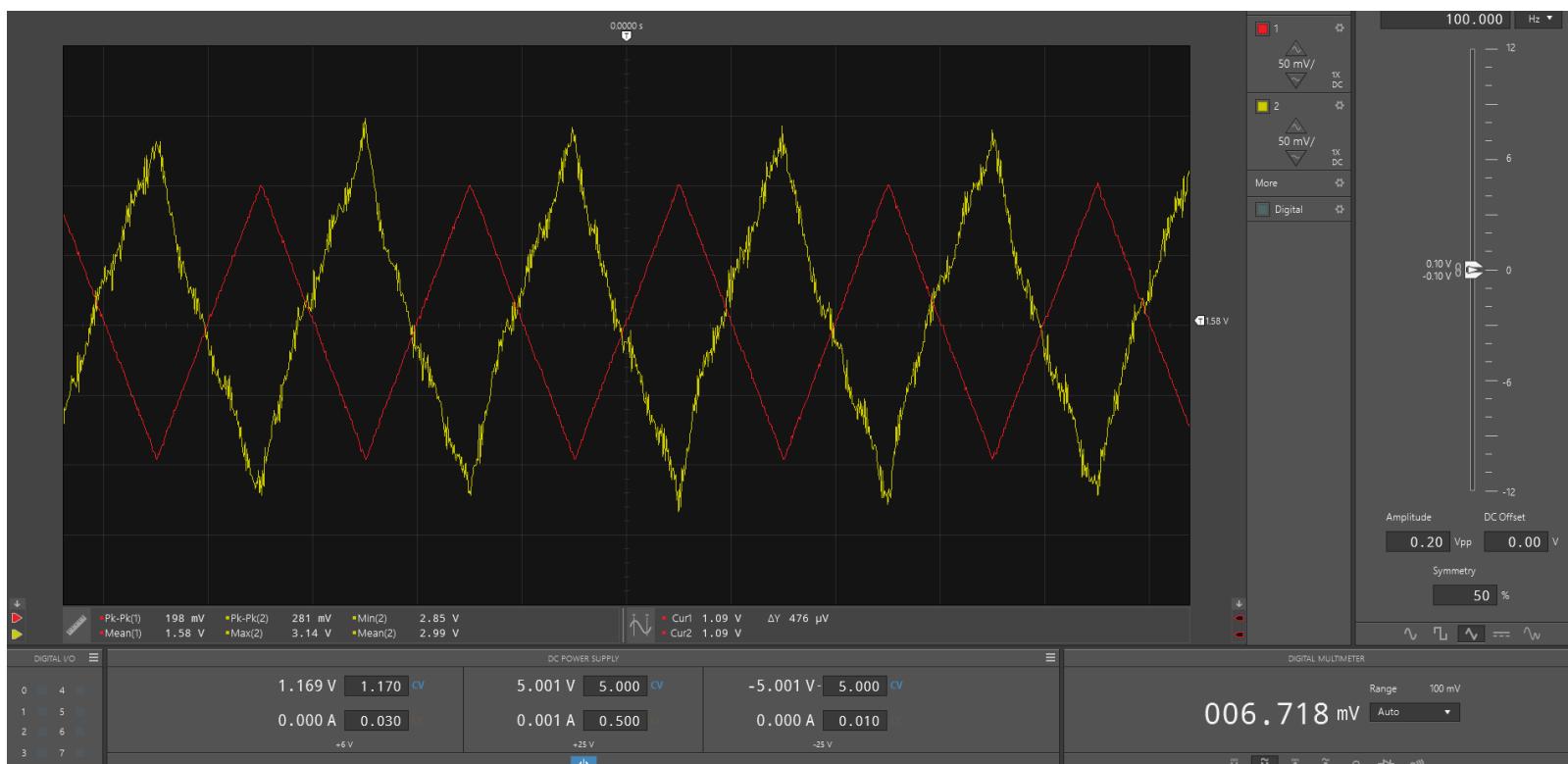

## CONCLUSION:

### ITEM 1:

Final schematic:

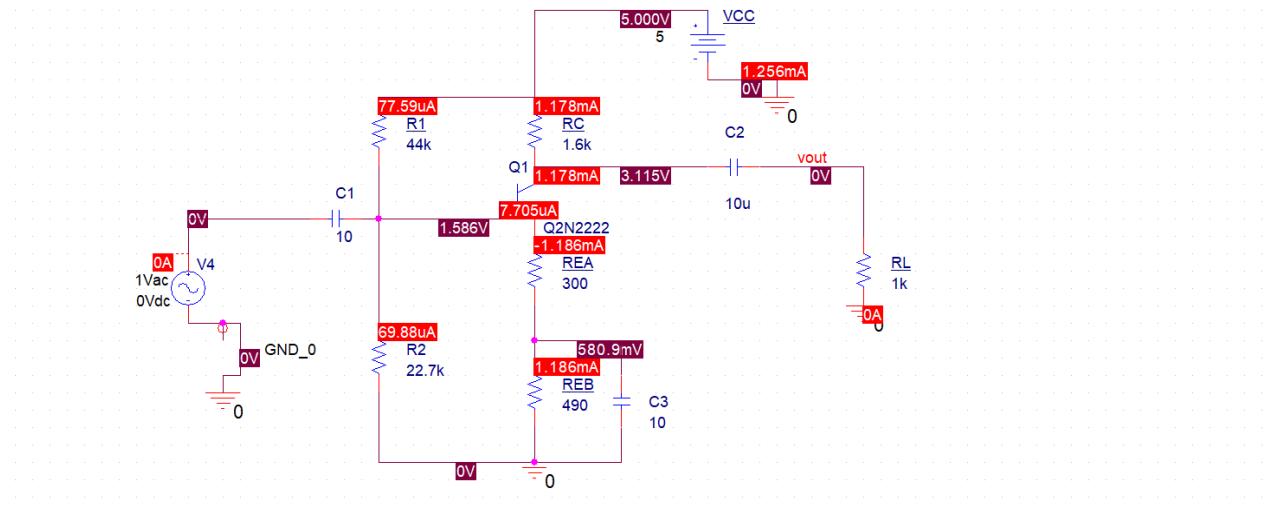

The state the collector current: is seen in step 8. Collector current =  $2.99/(1.6 \times 10^3)$  = 1.86mA

Value of Vbb:  $1 + 0.7 = 1.7V$

**ITEM 2:** To justify that our amplifier circuit has bias stability against variations of B  
Beta can be seen in the pspice temperature simulations.